

DSD LAB

Week 2

Udeet Mittal

CSE C3

Roll Number 64

Exercise:

Write behavioral Verilog code to implement the following and simulate


1. Full adder
2. Four-bit adder/ subtractor
3. Single-digit BCD adder using a four-bit adder(s).

1.

Source Code:

```
module fulladder(Cin,x,y,s,Cout);  
input Cin,x,y;  
output s,Cout;  
assign s = x ^ y ^ Cin;  
assign Cout = (x & y) | ( x & Cin) | ( y & Cin);  
endmodule
```

Output Waveform:

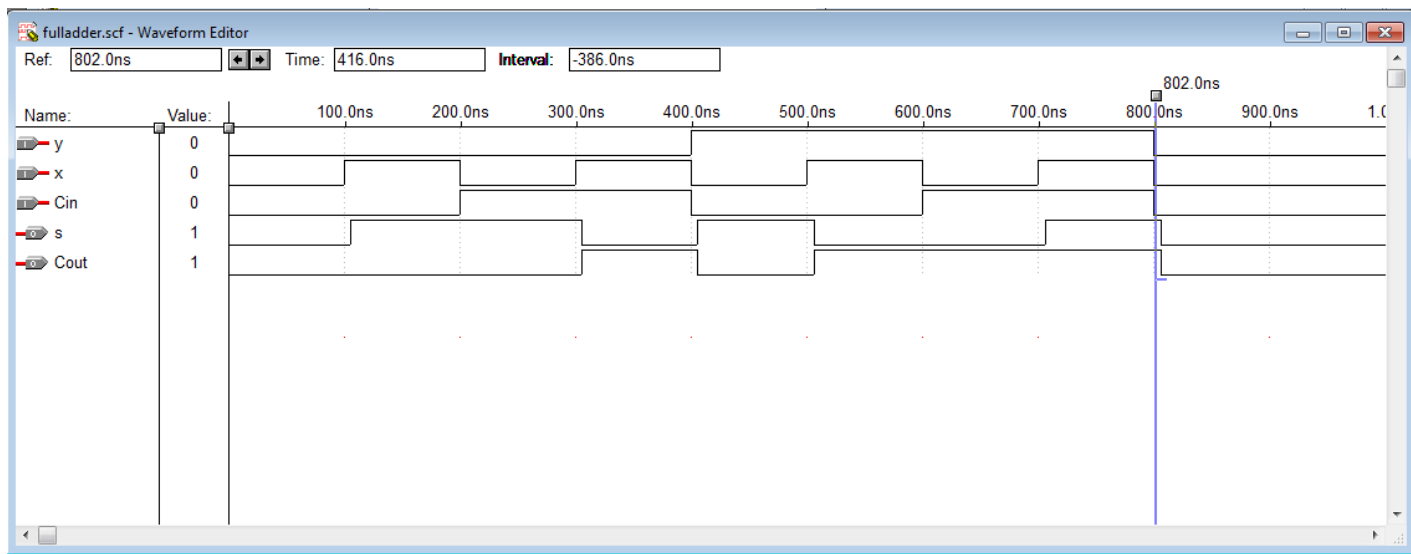

2.

Source Code:


```

module fourbitadder(carryin,x,y,s,carryout);
input carryin;
input[3:0] x,y;
output[3:0] s;
output carryout;
wire[3:1] C;
fulladder stage0(carryin , x[0] , y[0] ^ carryin , s[0] , C[1]);
fulladder stage1(C[1] , x[1] , y[1] ^ carryin , s[1] , C[2]);
fulladder stage2(C[2] , x[2] , y[2] ^ carryin , s[2] , C[3]);
fulladder stage3(C[3] , x[3] , y[3] ^ carryin , s[3] , carryout);
endmodule

//using the previous full adder module

```

Output Waveform:

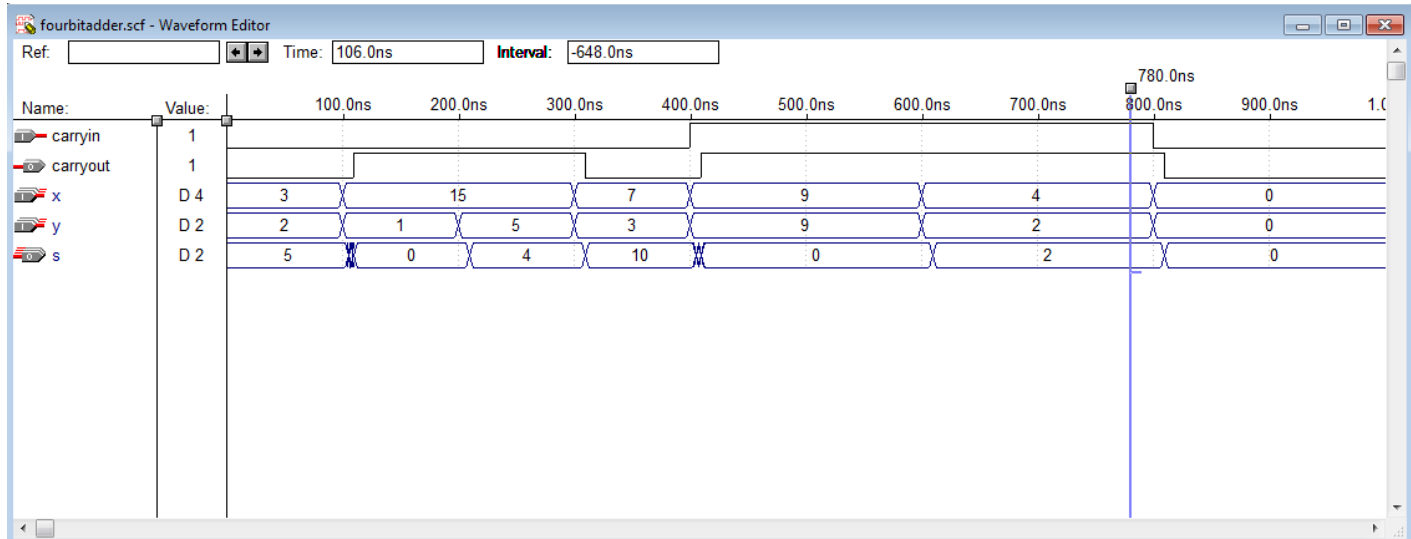

3.

Source Code:

```
module bcdadder(carryin,a,b,sum,carryout);  
input [3:0] a,b;  
input carryin;  
output [3:0]sum;  
output carryout;  
wire [3:0]z;  
wire c4,c41;  
wire [3:0]ss;  
fourbitadder stage1(carryin,a,b,z,c4);
```

```

assign carryout= (c4|(z[3] & z[2])|(z[3] & z[1]));
assign ss[0] = 1'b0;
assign ss[1] = carryout;
assign ss[2] = carryout;
assign ss[3] = 1'b0;
fourbitadder stage2(0,ss,z,sum,c4);
endmodule

```

Output Waveform:

